

4.1 For an NMOS differential pair with a common-mode voltage V_{CM} applied, as shown in Fig. 4.1, let $V_{DD} = 2V$, $\mu_n C_{ox} = 0.4 \text{ mA/V}^2$, $(W/L)_{1,2} = 10$, $V_{TH} = 0.4 \text{ V}$, $I_{SS} = 0.16 \text{ mA}$, $R_D = 5 \text{ k}\Omega$, and neglect channel-length modulation and body effect.

- Find V_{OD} and V_{GS} for each transistor.
- For $V_{CM} = 1V$, find V_P , I_{D1} , I_{D2} , V_{OUT1} , and V_{OUT2} .
- Repeat (b) for $V_{CM} = 1.4 \text{ V}$.
- Repeat (b) for $V_{CM} = 0.9 \text{ V}$.
- What is the highest value of V_{CM} for which M_1 and M_2 remain in saturation?
- If current source I_{SS} requires a minimum voltage of 0.2 V to operate properly, what is the lowest value allowed for V_P and hence for V_{CM} ?
- Find the small-signal differential gain under the condition of (b).

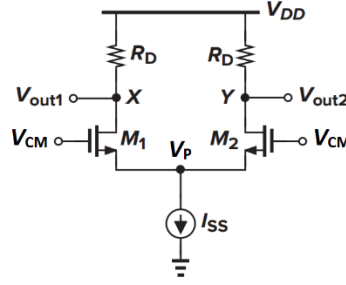


Fig. 4.1

(a)

$$\begin{aligned} \frac{I_{ss}}{2} &= \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_{1,2} V_{od}^2 \Rightarrow V_{od} = 0.2 \text{ V} \\ V_{GS} &= V_{od} + V_{th} = 0.6 \text{ V} \end{aligned} \quad (1-1)$$

(b) 假设处于饱和区

$$\begin{aligned} V_P &= V_{CM} - V_{GS} = 1 - 0.6 = 0.4 \text{ V} \\ I_{D1} &= I_{D2} = \frac{I_{SS}}{2} = 0.08 \text{ mA} \\ V_{OUT1} &= V_{OUT2} = V_{DD} - I_{D1,2} R_D = 2 - 0.4 = 1.6 \text{ V} \\ V_{DS} &= V_{OUT} - V_P = 1.6 - 0.4 = 1.2 \text{ V} > V_{od} \end{aligned} \quad (1-2)$$

假设正确

(c) 假设处于饱和区

$$\begin{aligned} V_P &= V_{CM} - V_{GS} = 1.4 - 0.6 = 0.8 \text{ V} \\ I_{D1} &= I_{D2} = \frac{I_{SS}}{2} = 0.08 \text{ mA} \\ V_{OUT1} &= V_{OUT2} = V_{DD} - I_{D1,2} R_D = 2 - 0.4 = 1.6 \text{ V} \\ V_{DS} &= V_{OUT} - V_P = 1.6 - 0.8 = 0.8 \text{ V} > V_{od} \end{aligned} \quad (1-3)$$

假设正确

(d) 假设处于饱和区

$$\begin{aligned} V_P &= V_{CM} - V_{GS} = 0.9 - 0.6 = 0.3 \text{ V} \\ I_{D1} &= I_{D2} = \frac{I_{SS}}{2} = 0.08 \text{ mA} \\ V_{OUT1} &= V_{OUT2} = V_{DD} - I_{D1,2} R_D = 2 - 0.4 = 1.6 \text{ V} \\ V_{DS} &= V_{OUT} - V_P = 1.6 - 0.3 = 1.3 \text{ V} > V_{od} \end{aligned} \quad (1-4)$$

假设正确

(e)

$$V_{CM} \leq V_{OUT1,2} + V_{TH} = 2 \text{ V} \quad (1-5)$$

(f)

$$\begin{aligned} V_P &\geq 0.2 \text{ V} \\ V_{CM} &\geq V_{P\min} + V_{GS} = 0.2 + 0.6 = 0.8 \text{ V} \end{aligned} \quad (1-6)$$

(g)

$$\begin{aligned} A_V &= -g_m R_D = -4 \\ g_m &= \sqrt{2I_{1,2}\mu_n C_{ox} \left(\frac{W}{L}\right)_{1,2}} = \frac{1}{1250} \text{ S} \end{aligned} \quad (1-7)$$

4.2 Consider the differential amplifier specified in Problem 4.1 with gate voltage of M2, V_{G2} , fixed to $V_{CM}=1\text{V}$, and V_{G1} is set to $V_{CM} + v_{id}$. Let v_{id} be adjusted to the value that causes $I_{D1}=0.09 \text{ mA}$ and $I_{D2}=0.07 \text{ mA}$.

- Find the corresponding values of V_{GS2} , V_P , V_{GS1} , and hence v_{id} .
- What is the difference output voltage $v_{od} = V_{out2} - V_{out1}$?
- What is the voltage gain v_{od}/v_{id} ? Explain the reason why the gain obtained here is different with that obtained in 4.1 (g).
- What value of v_{id} results in $I_{D1} = 0.07 \text{ mA}$ and $I_{D2} = 0.09 \text{ mA}$?
- What is the maximum range of v_{id} that ensures either I_{D1} or I_{D2} be larger than 0.

(a)

$$\begin{aligned} V_{GS1} &= \sqrt{\frac{2I_{D1}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1}} + V_{TH} = 0.212 + 0.4 = 0.612 \text{ V} \\ V_{GS2} &= \sqrt{\frac{2I_{D2}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_2}} + V_{TH} = 0.187 + 0.4 = 0.587 \text{ V} \\ V_P &= V_{G1} - V_{GS1} = 1 - 0.612 = 0.388 \text{ V} \\ v_{id} &= V_{GS1} - V_{GS2} = 0.612 - 0.587 = 0.025 \text{ V} \end{aligned} \quad (2-1)$$

(b)假设处于饱和区

$$\begin{aligned} V_{OUT1} &= V_{DD} - I_{D1} R_D = 2 - 0.45 = 1.55 \text{ V} \\ V_{OUT2} &= V_{DD} - I_{D2} R_D = 2 - 0.35 = 1.65 \text{ V} \\ v_{od} &= V_{OUT1} - V_{OUT2} = 0.1 \text{ V} \end{aligned} \quad (2-2)$$

处于饱和区假设成立

(c)

$$\frac{v_{od}}{v_{id}} = \frac{0.1}{0.025} = 4 \quad (2-3)$$

(d)

$$v_{id} = -0.025 \text{ V} \quad (2-4)$$

(e)

$$v_{id} \leq \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_{1,2}}} = 0.28 \text{ V} \quad (2-5)$$

4.3 Fig. 4.3 shows a MOS differential amplifier with the drain resistors R_D implemented using diode-connected PMOS transistors, M3 and M4. Let M1 and M2 be matched, and M3 and M4 be matched. Neglect body effect.

- Draw the differential half-circuit and use it to derive an expression for A_{DM} in terms of $g_{m1,2}$, $g_{m3,4}$, $r_{o1,2}$, and $r_{o3,4}$.
- Neglecting the effect of the output resistances r_o , find A_{DM} in terms of $\mu_n C_{ox}$, $\mu_p C_{ox}$, $(W/L)_{1,2}$ and $(W/L)_{3,4}$.
- With the condition of (b), if $\mu_n = 4\mu_p$ and all four transistors have the same channel length, find $(W_{1,2}/W_{3,4})$ that results in $A_{DM} = 10$ V/V.
- Find the maximum $V_{in,CM}$ that ensures saturation of M1 and M2 in terms of V_{DD} , I_{SS} , $\mu_p C_{ox}$, $(W/L)_{3,4}$, V_{THP} and V_{THN} .

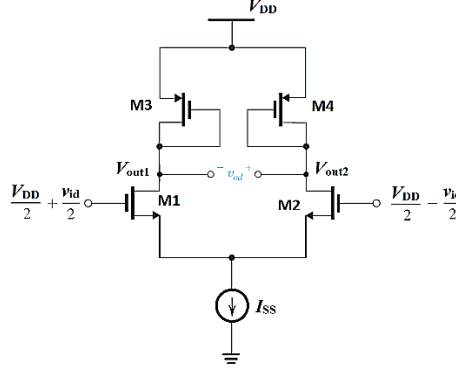


Fig. 4.3

(a)

等效电路略

$$A_{DM} = g_{m1,2} \left(\frac{1}{g_{m3,4}} \parallel r_{o3,4} \parallel r_{o1,2} \right) \quad (3-1)$$

(b)

$$A_{DM} = \frac{g_{m1,2}}{g_{m3,4}} = \sqrt{\frac{\mu_n C_{ox} \left(\frac{W}{L} \right)_{1,2}}{\mu_p C_{ox} \left(\frac{W}{L} \right)_{3,4}}} \quad (3-2)$$

(c)

$$10 = 2 \sqrt{\frac{W_{1,2}}{W_{3,4}}} \Rightarrow \frac{W_{1,2}}{W_{3,4}} = 25 \quad (3-3)$$

(d)

$$V_{in,CM} \leq V_{OUT} + V_{TH1,2} = V_{DD} - V_{od3,4} + V_{TH1,2} = V_{DD} - \sqrt{\frac{I_{SS}}{\mu_p C_{ox} \left(\frac{W}{L} \right)_{3,4}}} + V_{THN} \quad (3-4)$$

(e)

4.4 For the differential amplifier shown in Fig. 4.4, neglect the channel length modulation effect.

- (a) Draw the differential half-circuit for the amplifier and use it to derive an expression for the differential gain $A_{DM} \equiv v_{od}/v_{id}$ in terms of g_m , R_D , and R_S .
- (b) What is the gain with $R_S = 0$?
- (c) What is the value of R_S (in terms of $1/g_m$) that reduces the gain to half of value at $R_S = 0$?
- (d) Derive the maximum range of v_{id} (in terms of g_m , I_{SS} , R_S) that ensures either I_{D1} or I_{D2} be larger than 0.


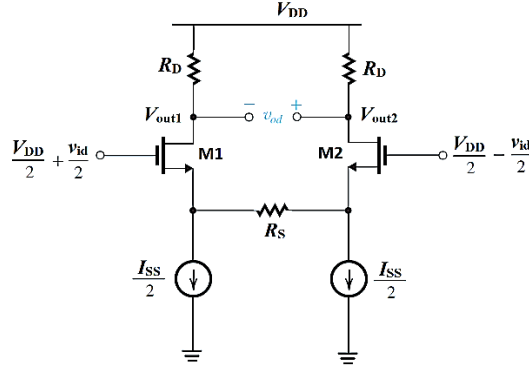


Fig. 4.4

- (a) 见ppt39页

$$A_v = \frac{g_{m1} R_D}{1 + g_{m1} R_S/2} \quad (4-1)$$

- (b) 短路为基础的差动放大器

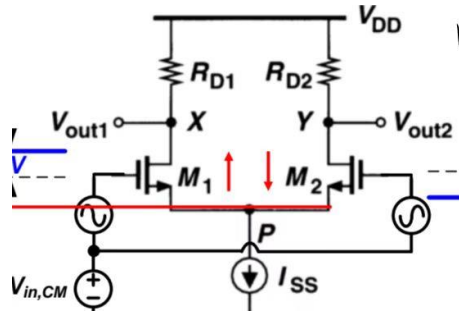

$$A_v = g_{m1} R_D \quad (4-2)$$

- (c)

$$R_S = 2/g_m \quad (4-3)$$

- (d) V_{in1} 刚好截止时,

$$V_{in1} - V_P = V_{TH} \quad (4-4)$$

此时 V_{in2} 流过两路电流,

$$V_{in2} - V_P = R_S \times \frac{I_{SS}}{2} + V_{TH} + \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} \quad (4-5)$$

相减可得

$$|V_{in1} - V_{in2}| = \frac{R_S I_{SS}}{2} + \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} = \frac{R_S I_{SS}}{2} + \sqrt{2} \cdot V_{OD} \quad (4-6)$$

4.5 A design error has resulted in a gross mismatch in the circuit of Fig. 4.5. Specifically, M2 has twice the W/L ratio of M1. Neglect channel length modulation effect and body effect. If v_{id} is a small AC signal, find:

- I_{D1} and I_{D2} for $v_{id}=0$.
- The offset voltage, $v_{od,offset}$, at the output nodes. (Hint: $v_{od,offset}=V_{out1}-V_{out2}$ when $v_{id}=0$.)
- V_{OD} for each of M1 and M2 in terms of I_{SS} , W/L and $\mu_n C_{ox}$.
- The differential gain A_{DM} in terms of R_D , I_{SS} , and V_{OD} . (Note: you cannot use the half-circuit method as the circuit is asymmetrical)

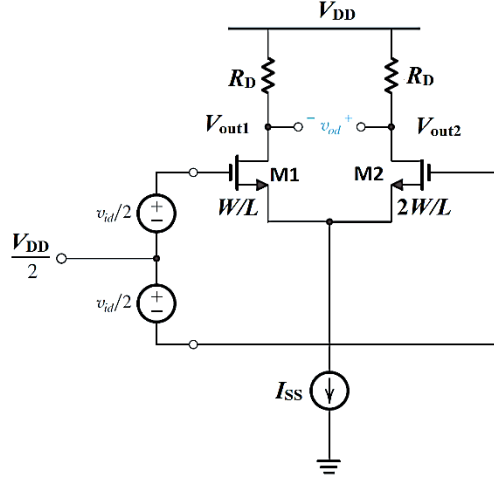


Fig. 4.5

(a)

$$\begin{cases} I_2 = 2I_1 \\ I_1 + I_2 = I_{SS} \end{cases} \Rightarrow \begin{cases} I_1 = \frac{1}{3} I_{SS} \\ I_2 = \frac{2}{3} I_{SS} \end{cases} \quad (5-1)$$

(b)

$$v_{od,offset} = (I_2 - I_1) R_D = \frac{1}{3} I_{SS} R_D \quad (5-2)$$

(c)

$$\begin{aligned} V_{od1} &= \sqrt{\frac{2I_1}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1}} = \sqrt{\frac{2I}{3\mu_n C_{ox} \left(\frac{W}{L}\right)_1}} \\ V_{od2} &= \sqrt{\frac{2I_2}{\mu_n C_{ox} \left(\frac{W}{L}\right)_2}} = \sqrt{\frac{4I}{3\mu_n C_{ox} \left(\frac{W}{L}\right)_2}} \end{aligned} \quad (5-3)$$

(d)

$$\begin{aligned} A_{DM} &= \frac{2R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}} \\ g_{m1} &= \frac{2I_1}{V_{OD1}} = \frac{2I_{SS}}{3V_{OD1}} \\ g_{m2} &= \frac{2I_2}{V_{OD2}} = \frac{4I_{SS}}{3V_{OD2}} \end{aligned} \quad (5-4)$$

$$\begin{aligned} A_{CM-DM} &= \frac{\Delta g_m R_D}{1 + 2g_m R_{SS}} = 1.3178 \times 10^{-3} \\ CMRR &= \frac{g_m R_D}{\frac{\Delta g_m R_D}{1 + 2g_m R_{SS}}} = \frac{g_m}{\Delta g_m} (1 + 2g_m R_{SS}) = 4292.66 = 72.65 \text{ dB} \end{aligned} \quad (6-3)$$